
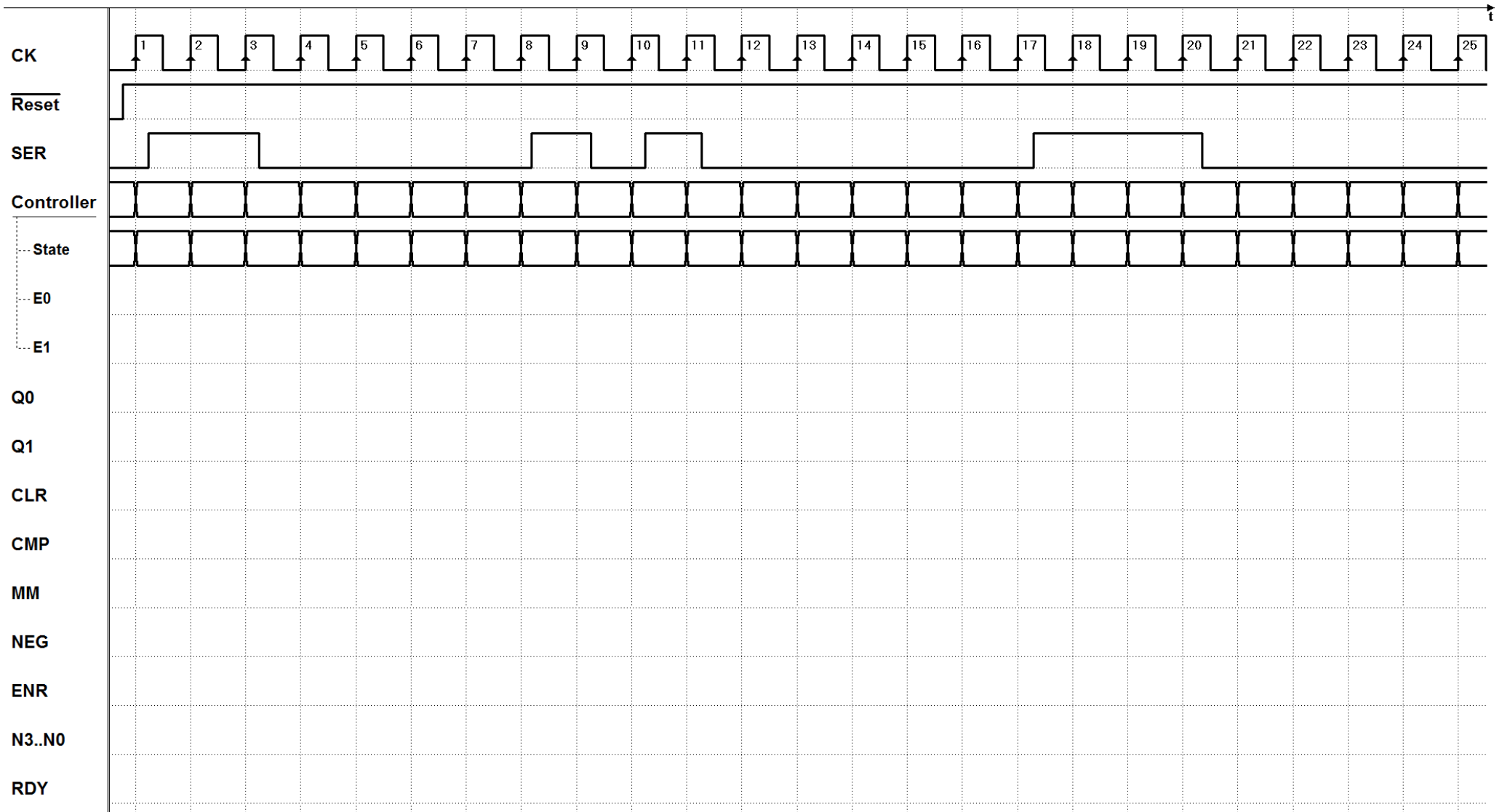


Chapter 8 – Exercise 3 – Design of the controller of a given datapath – Timing diagram to be completed

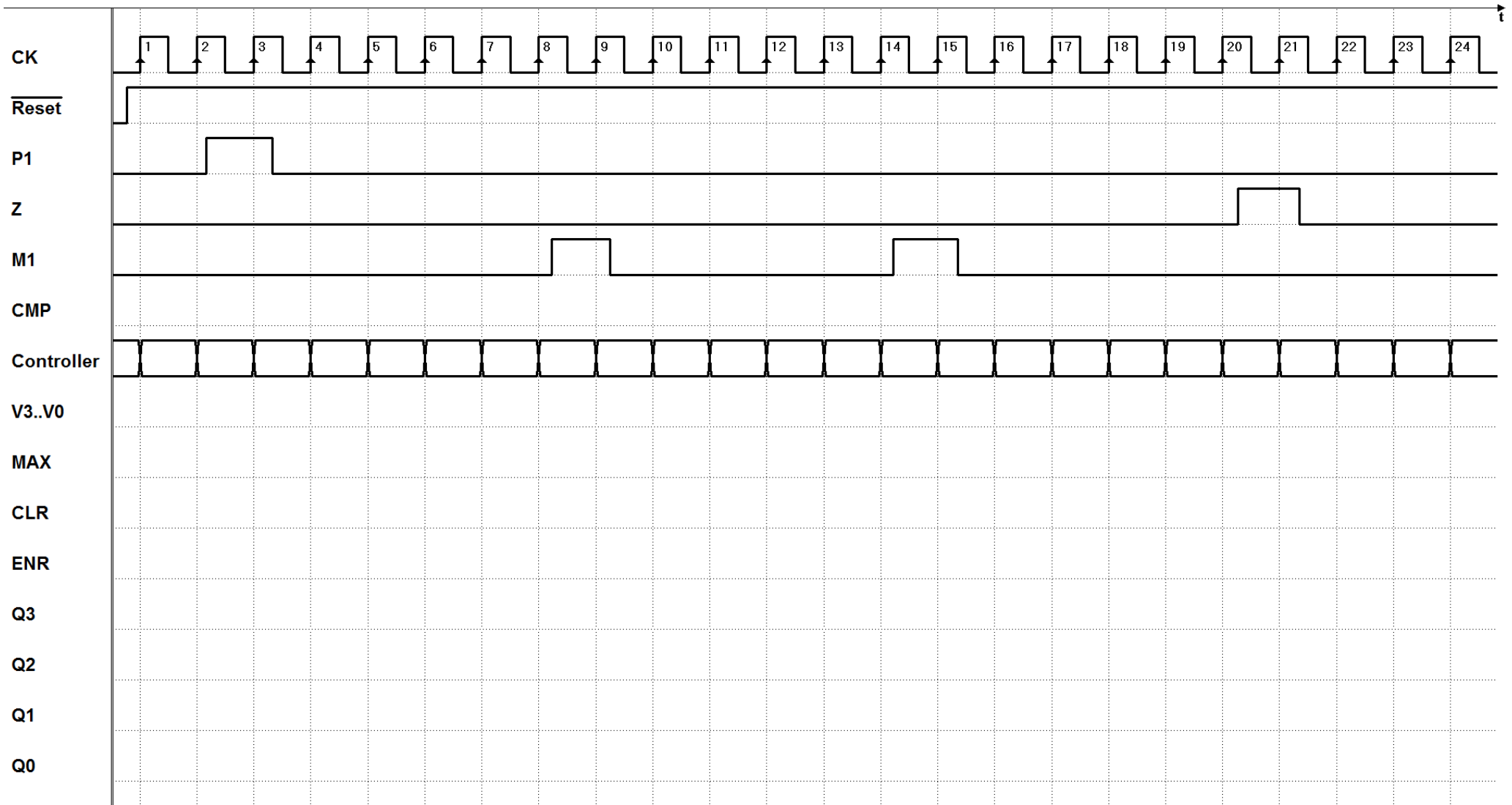

Chapter 8 – Exercise 4 – Design of the controller of a given datapath – Timing diagram to be completed



Chapter 8 – Exercise 5 – Design of the controller of a given datapath – Timing diagram to be completed

